

-071

**SOUTH EASTERN UNIVERSITY OF SRI LANKA**  
**FIRST EXAMINATION IN BACHELOR OF INFORMATION AND**  
**COMMUNICATION TECHNOLOGY - 2019/2020**  
**SEMESTER – I, AUGUST - 2022**

**CIS11032- Logic Designing and Computer Organization**

**Answer all Questions**

**Time: 02 hours.**

**Question 01:**

- a) What is a computer? And discuss the components of the computer by relating the human body parts. (20 Marks)
- b) Explain how the audio data can be stored on a computer. (20 Marks)
- c) What is **radix/base** in number system and why it is used? (10 Marks)
- d) Differentiate between the positional and non-positional number systems by mentioning some examples. (20 Marks)
- e) Convert the following decimal fraction into binary, octal and hexadecimal.
  - i. 12.03
  - ii. 9.325(30 Marks)

[Total 100 marks]

**Question 02:**

- a) Convert the following numbers into decimal number.
  - i.  $1BCD4.54_{16}$
  - ii.  $1663_8$
  - iii.  $1110011.001_2$(15 Marks)
- b) Transform the following octal and hexadecimal numbers into binary number and convert the given binary number into octal and hexadecimal numbers.
  - i.  $371.2_8$
  - ii.  $3DCA.31A_{16}$
  - iii.  $1001011110.110_2$(15 Marks)
- c) List out and briefly describe the three ways in which signed binary numbers can be expressed. (15 Marks)
- d) Add  $17_{10}$  to  $-8_{10}$  using **one's complement** arithmetic and verify your answer. (10 Marks)
- e) Calculate the **two's complement** of  $-174_{10}$  (10 Marks)
- f) Find the decimal equivalent of the 8-bit 2's complement value  $1100111010_2$ . (15 Marks)
- g) Explain the following gates using a suitable diagram.
  - i. AND gate
  - ii. OR gate(20 Marks)

[Total 100 marks]


**Question 03:**

a) What is **truth table** and construct truth table for the following Boolean expression.

- $(XYZ) + (\bar{X} + Y)$
- $(A + \bar{B})(AB + \bar{C})$

(25 Marks)

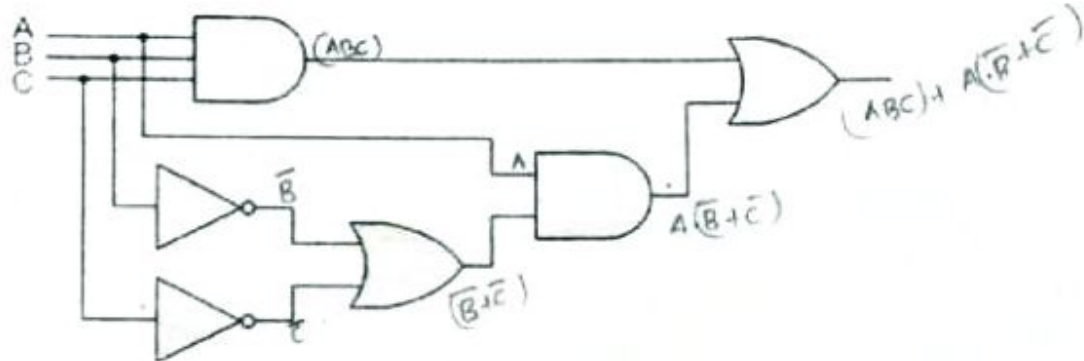b) Convert the following logic gate circuit into a **Boolean Expression** and **truth table**



(20 Marks)

c) Derive a Boolean expressions from the given truth table.

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(15 Marks)

d) Minimize the following Boolean function using **Karnaugh maps**.


- $B, C, D) = \sum m(3, 4, 5, 7, 9, 13, 14, 15)$
- $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 10, 12, 15) + \sum d(3, 14)$

(40 Marks)

[Total 100 marks]

**Question 04:**

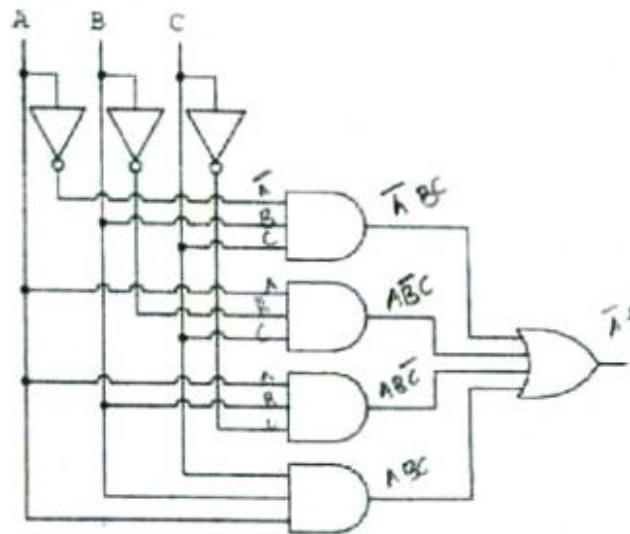- a) Simplify the output of the following logic gate circuit by converting it into Boolean expression and truth table.



(25 Marks)

- b) Discuss the components of the central processing unit (CPU).

(20 Marks)

- c) Describe how an ALU works.

(15 Marks)

- d) Simplify the following expressions using Boolean algebra.

- $AB + A(B + C) + B(B + C)$
- $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$
- $\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + ABC$
- $(A + \bar{B})(AB) + (A + B)(\bar{A}\bar{B})$

(40 Marks)

[Total 100 marks]

-----The End-----

AB	00	01	11	10
0				
1				

AB	00	01	11	10
0				
1				