

Department of Information and Communication Technology
Faculty of Technology
South Eastern University of Sri Lanka

Tutorial 02
Boolean Logic

Part A: Simplify using Laws of Boolean Algebra

1. $ABC + ABC' + AB'C + A'BC$
2. $AB + A'C + AB'C + BC$
3. $ABC + ABC' + A'B'C + AB'C$
4. $ABC + A'BC + AB'C' + ABC'$
5. $(A+B)(A+C) + A'BC$
6. $(AB + A'C) + (A+B)C$
7. $AB' + A(B+C)' + B(B+C)'$
8. $[AB'(C+BD) + A'B']C$
9. $A'BC + AB'C' + A'B'C' + AB'C + ABC$

Part B: Map the following expressions to a K-map and simplify. (Note: Convert to Standard SOP before mapping to a K-map)

1. $A'B'CD + A'BC'D' + ABC'D + ABC'D' + A'B'C'D + ABCD + AB'CD'$
2. $A' + AB' + ABC'$
3. $B'C' + AB' + ABC' + AB'CD' + A'B'C'D + AB'CD$
4. $F(A,B,C) = \sum(0,1,2,4,5,6)$
5. $F(A,B,C,D) = \sum(0,1,5,7,8,9,11,13) + \sum d(2,3)$

Part C: Construct Simple Logic Circuits

1. A room has three sensors:
A (Motion Sensor) – Detects if someone is in the room (1 = person detected, 0 = no one).
B (Daylight Sensor) – Detects if there is enough sunlight (1 = bright, 0 = dark).
C (Manual Switch) – Allows manual control (1 = ON, 0 = OFF).

Requirement:

The light should turn ON (Output = 1) if either:

Motion is detected AND it's dark.

The manual switch is turned ON.

2. A car has three sensors:

A (Seatbelt Sensor) – 1 if the seatbelt is not fastened.

B (Ignition Sensor) – 1 if the ignition is ON.

C (Weight Sensor) – 1 if a person is seated.

Requirement:

The warning alarm (Output = 1) should activate if:

A person is seated AND the ignition is ON AND the seatbelt is not fastened.

3. A farm uses a system to control a water pump based on three conditions:

A (Soil Moisture Sensor) – 1 if the soil is dry.

B (Rain Sensor) – 1 if it is raining.

C (Manual Switch) – 1 if the pump is turned on manually.

Requirement:

The pump should turn ON if:

The soil is dry AND it is not raining.

The manual switch is ON.